

Ahmad Malik

11/29/22

ECE-310

Lab4

Model #1: 4-bit register with synchronous reset and load

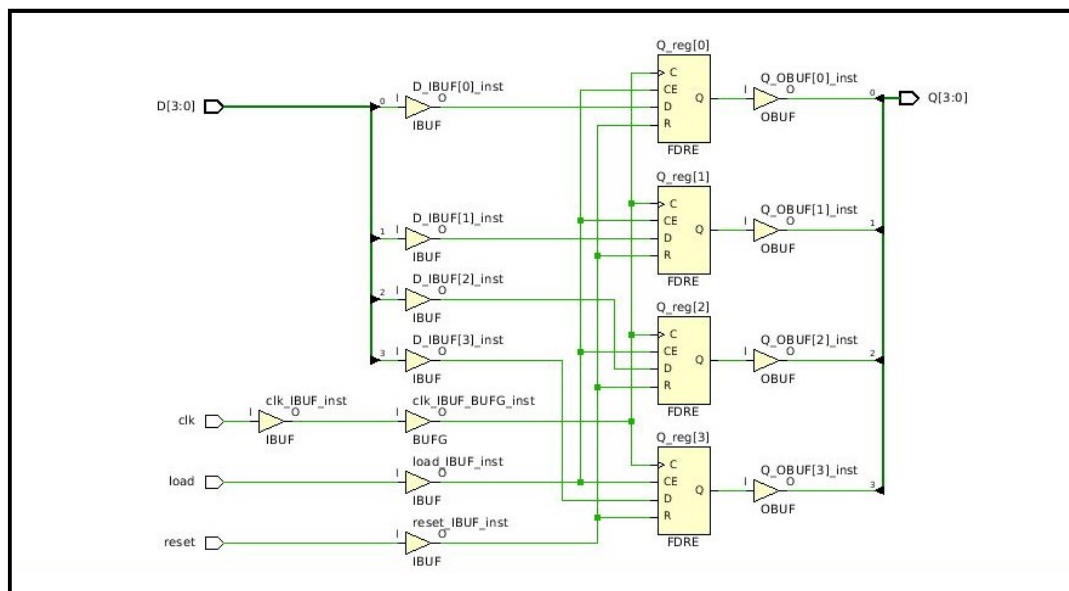


Figure 1: RTL Schematic of 4-bit register

 


Figure 2: Post-Implementation Timing simulation waveform. It is very similar to the behavioral Simulation waveform.

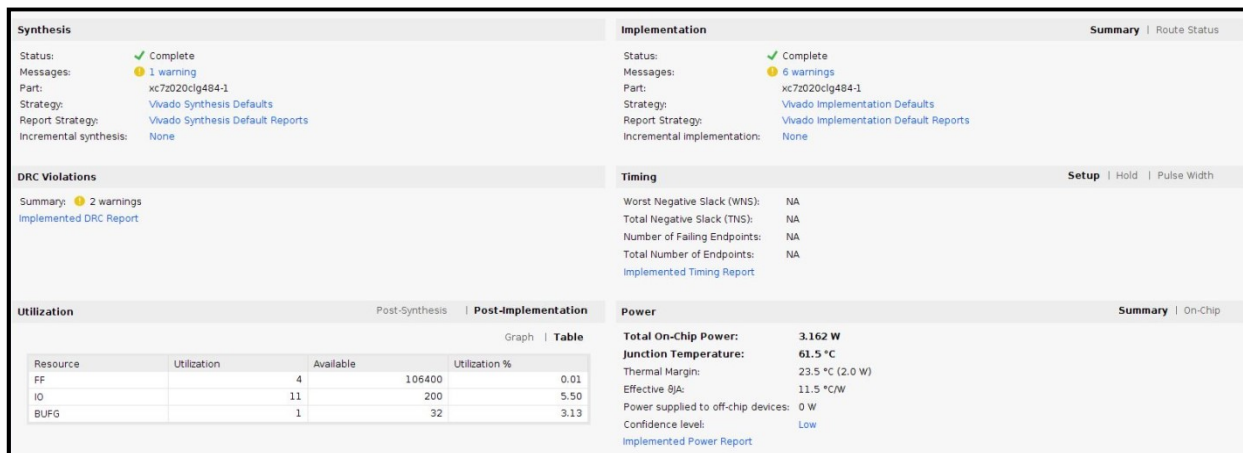


Figure 3: Project Summary and Utilization. Highest is IO.

Model #2: 4-bit parallel in left shift register

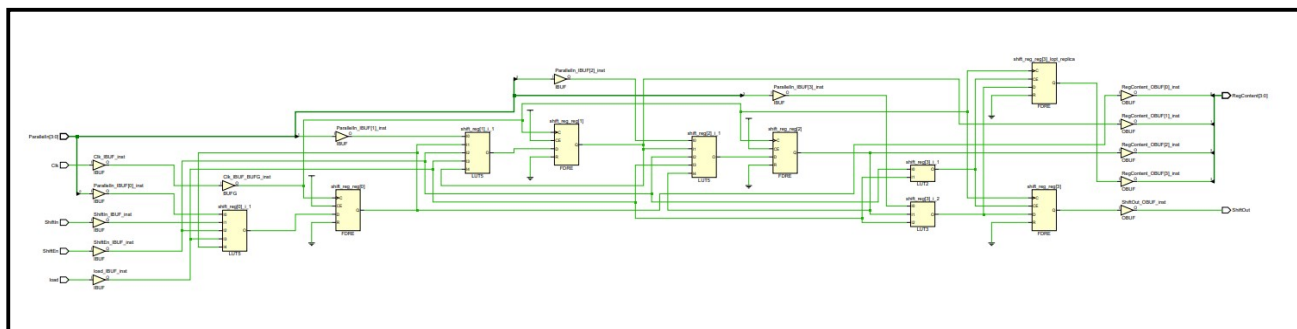


Figure 4: RTL Schematic of 4-bit parallel in left shift register

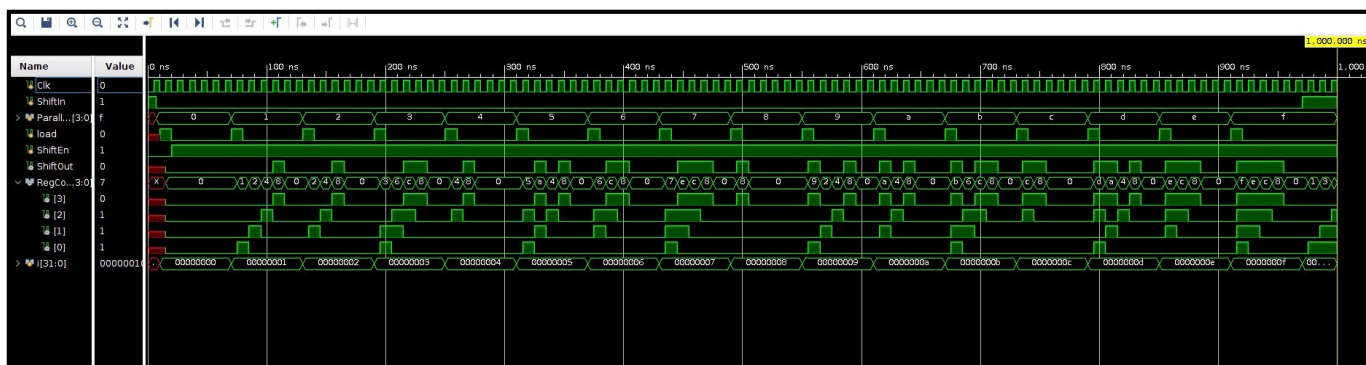


Figure 5: Post-Implementation Timing simulation waveform. Notice RegContent shifts the data as the clocks pulses

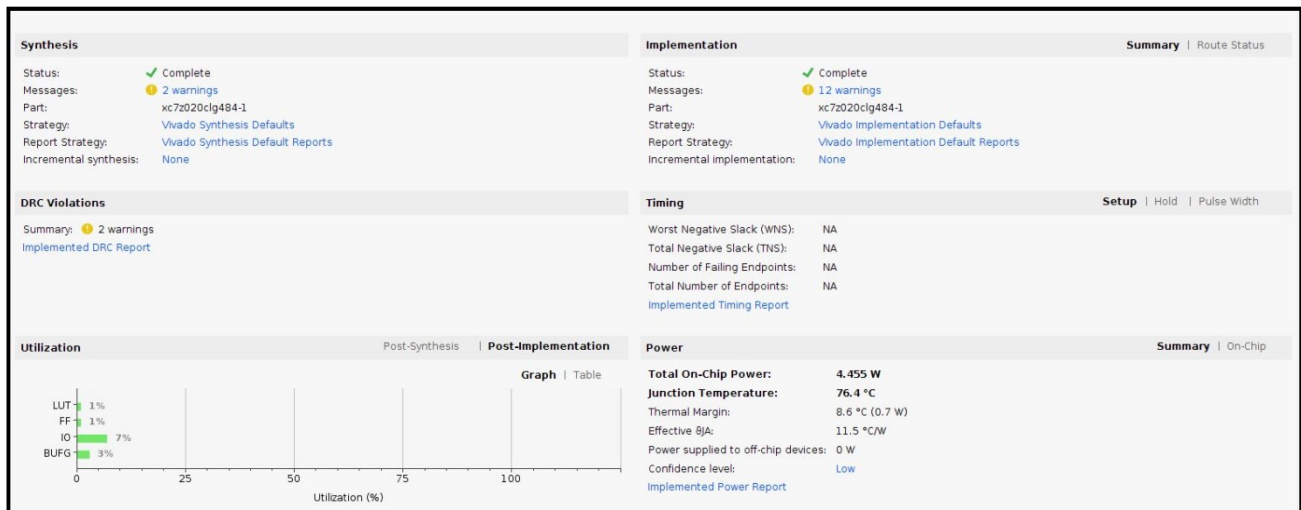


Figure 6: Project Summary and Utilization. Highest is IO with new utilization of LUT.

Model #3: 8-bit counter using T flip-flops

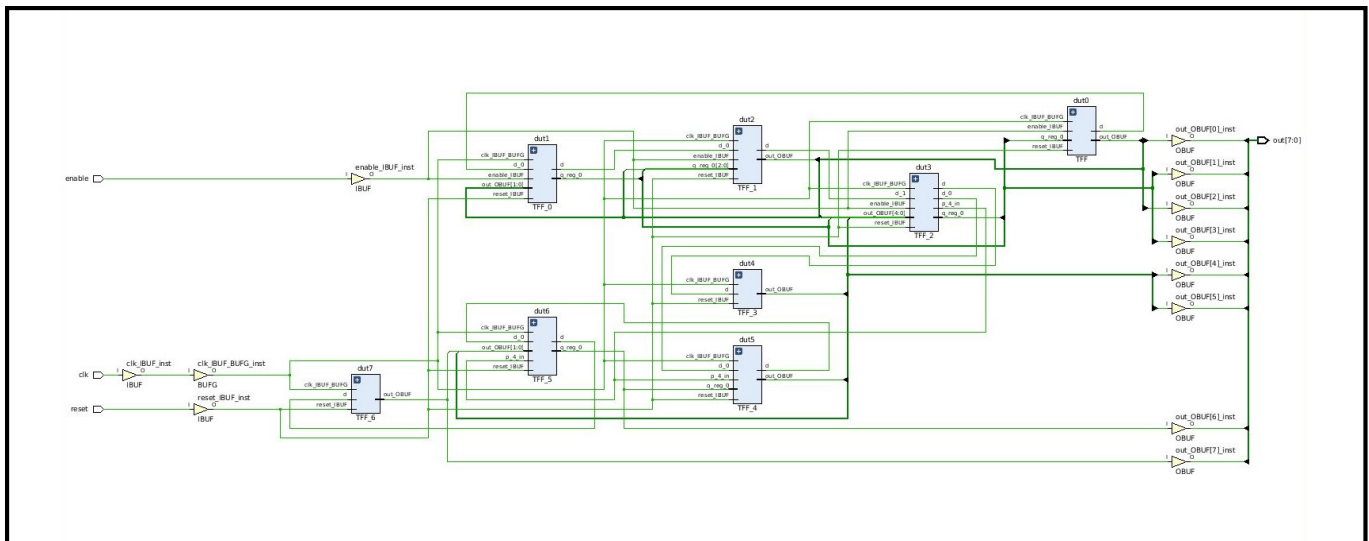


Figure 7: RTL Schematic of 8-bit counter using T flip-flops

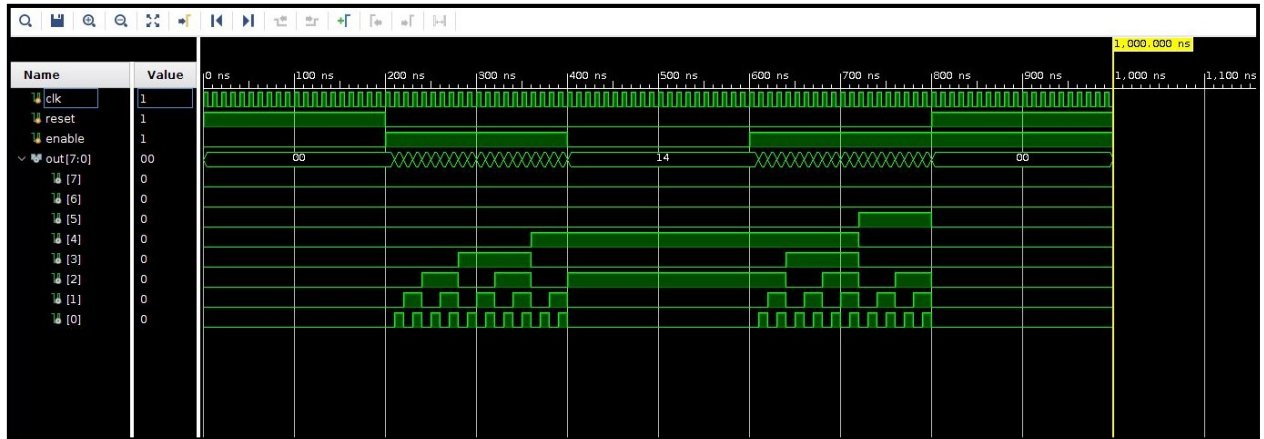


Figure 8: Post-Implementation Timing simulation waveform. Notice Counter value increases from 0 to 14 on positive edge of clock along with the enable and reset mode changes the output correspondingly

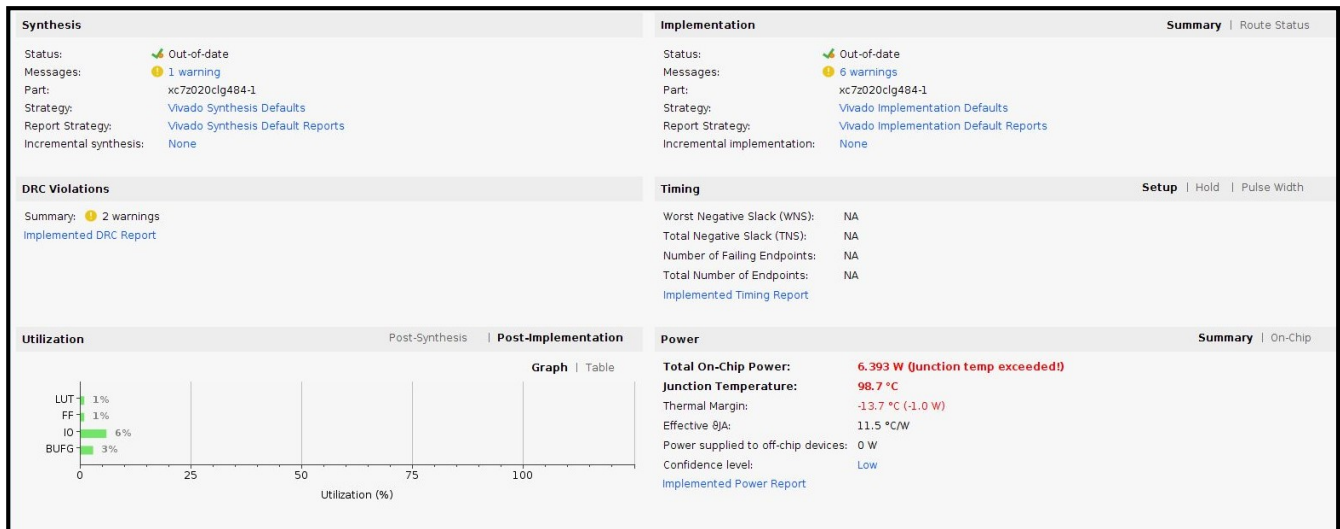


Figure 9: Project Summary and Utilization. Highest is IO and considerable power usage.

Model #4: 8-bit counter using D flip-flops

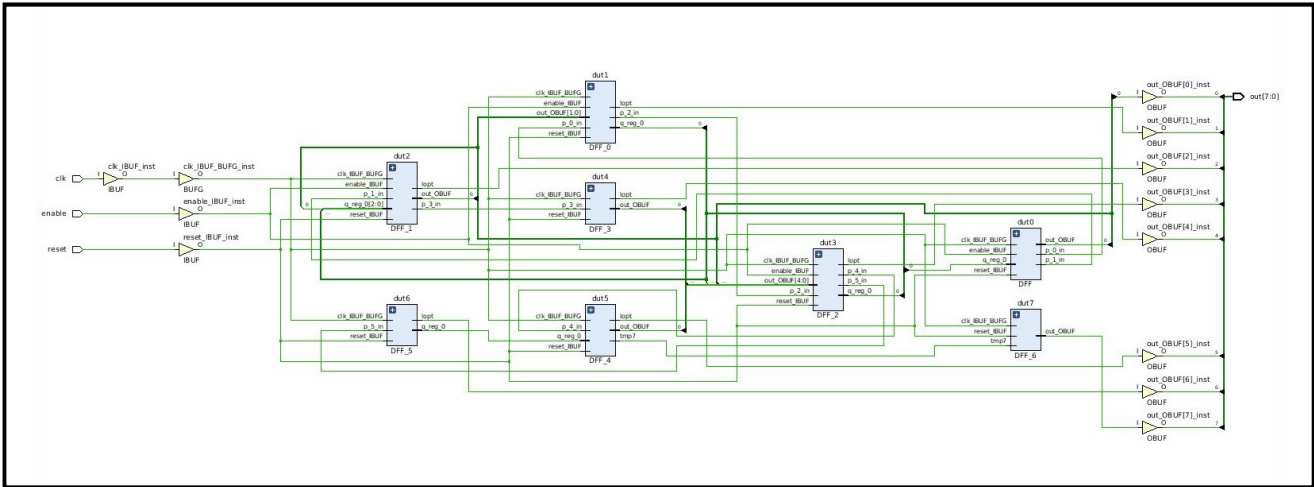


Figure 10: RTL Schematic of 8-bit counter using D flip-flops



Figure 11: Post-Implementation Timing simulation waveform.

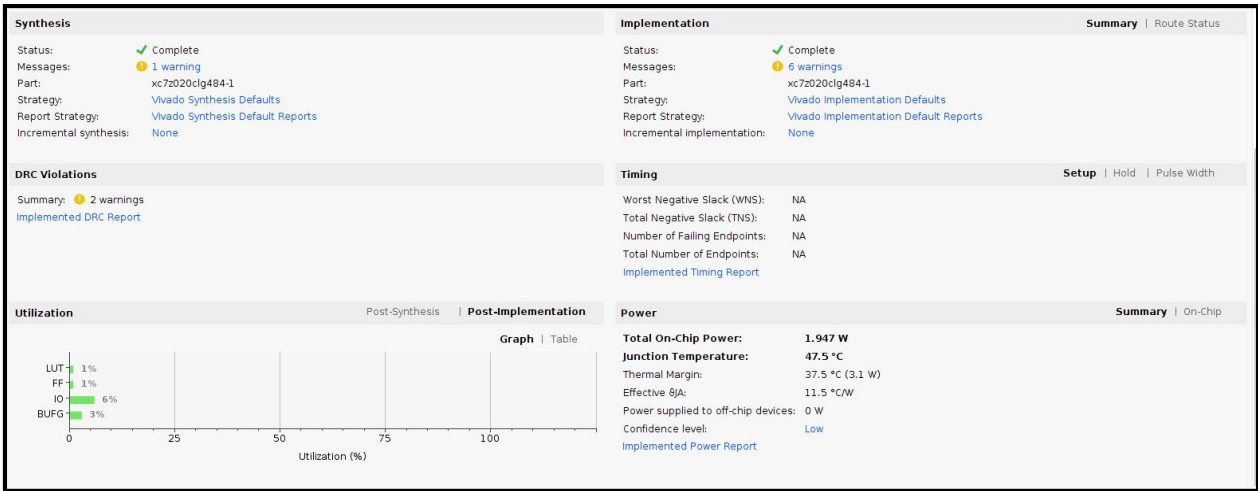


Figure 12: Project Summary and Utilization. Highest is IO and considerable power usage.

Model #5: Counter with sequence: 000, 001, 011, 101, 111, 010

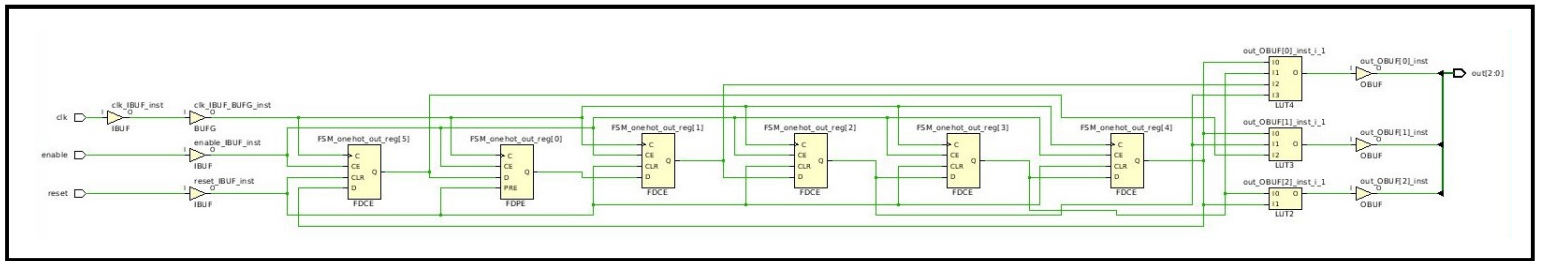


Figure 13: RTL Schematic of Counter

 


Figure 14: Post-Implementation Timing simulation waveform.


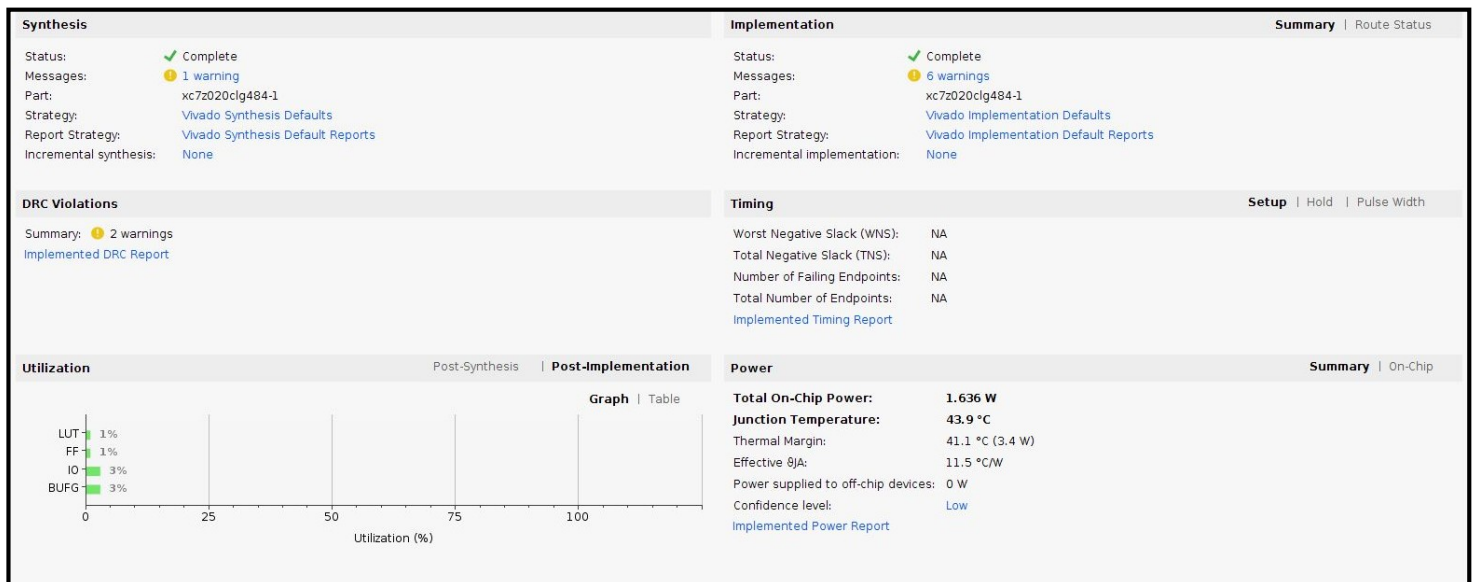
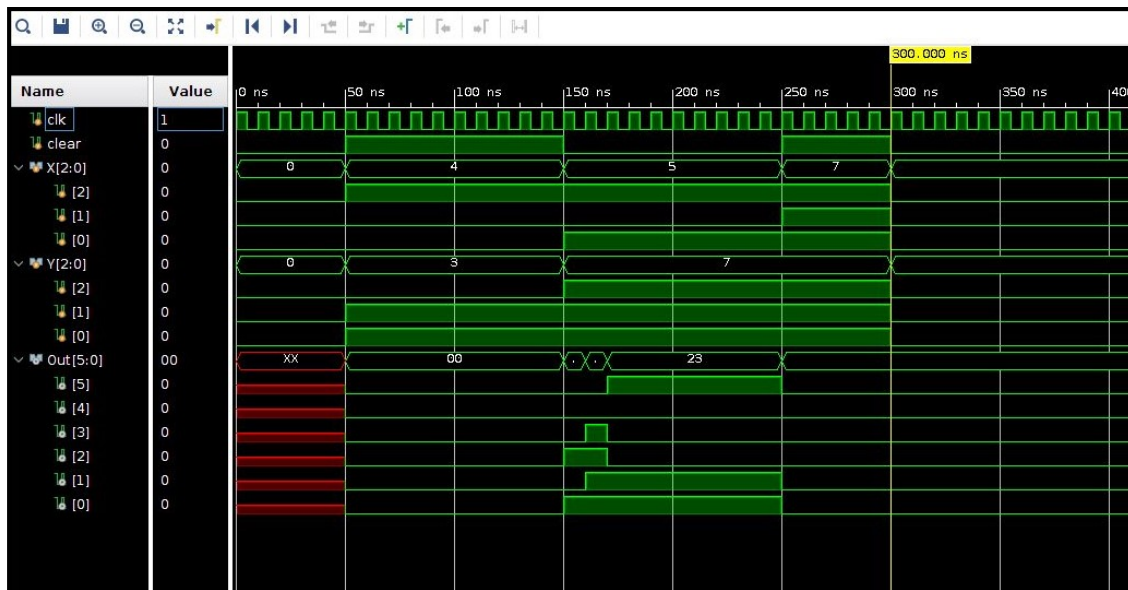


Figure 15: Project Summary and Utilization. Highest is IO and okay power usage.

Model #6: 3bit Multiplier

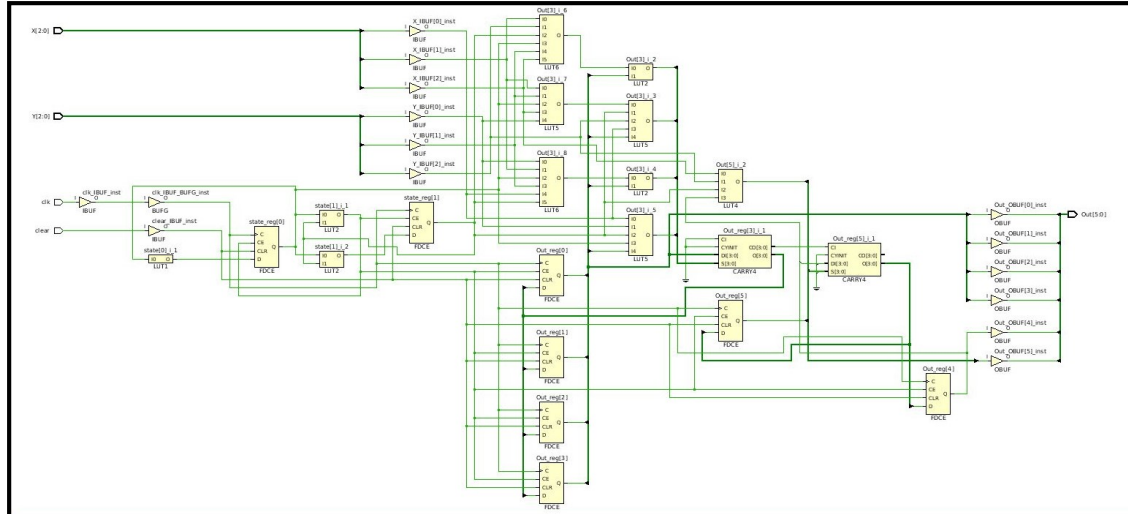

Synthesis		Implementation		Summary Route Status	
Status:	✔ Complete	Status:	✔ Complete		
Messages:	● 1 warning	Messages:	● 6 warnings		
Part:	xc7z020clg484-1	Part:	xc7z020clg484-1		
Strategy:	Vivado Synthesis Defaults	Strategy:	Vivado Implementation Defaults		
Report Strategy:	Vivado Synthesis Default Reports	Report Strategy:	Vivado Implementation Default Reports		
Incremental synthesis:	None	Incremental implementation:	None		
DRC Violations		Timing		Setup Hold Pulse Width	
Summary: ● 2 warnings Implemented DRC Report		Worst Negative Slack (WNS): NA Total Negative Slack (TNS): NA Number of Failing Endpoints: NA Total Number of Endpoints: NA Implemented Timing Report			
Utilization		Power		Summary On-Chip	
Post-Synthesis Post-Implementation		Total On-Chip Power: 8.456 W (Junction temp exceeded!)			
Graph Table		Junction Temperature: 122.5 °C			
		Thermal Margin: -37.5 °C (-2.6 W)			
Utilization (%)		Effective θJA: 11.5 °C/W			
		Power supplied to off-chip devices: 0 W			
		Confidence level: Low			
		Implemented Power Report			